
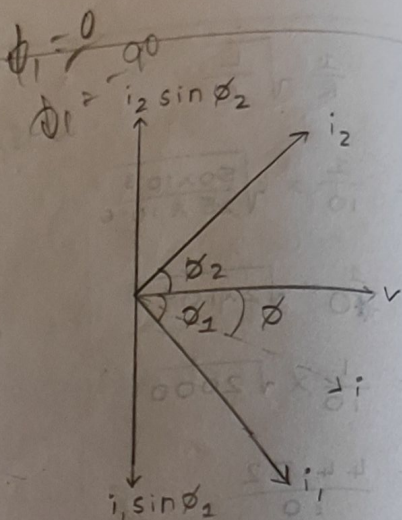


RLC in Parallel:

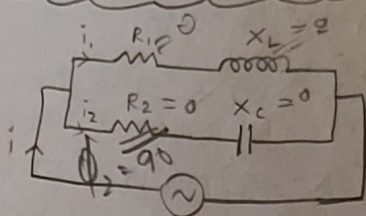

$$X = i_1 \cos \phi_1 + i_2 \cos \phi_2$$

$$Y = i_2 \sin \phi_2 - i_1 \sin \phi_1$$

$$i = \sqrt{X^2 + Y^2}$$

$$= \sqrt{(i_1 \cos \phi_1 + i_2 \cos \phi_2)^2 + (i_2 \sin \phi_2 - i_1 \sin \phi_1)^2}$$



$$\cos \phi_1 = \frac{R_1}{Z_1}$$

$$\cos \phi_2 = \frac{R_2}{Z_2}$$

$$Z_1 = \cos \phi R_1$$

$$\cos \phi = \frac{X}{Z}$$

$$\tan \phi = \frac{Y}{X}$$

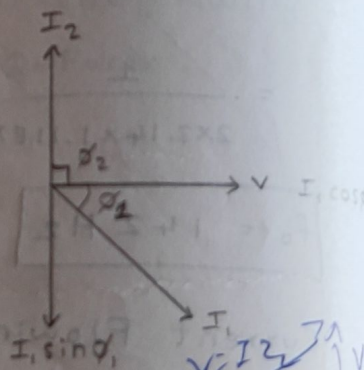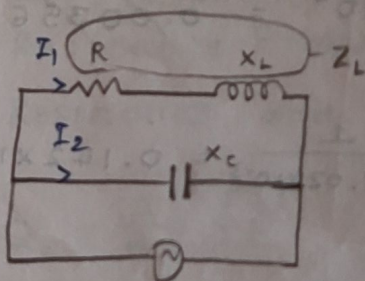

At resonance:

Sum of reactances = 0

$$I_2 - I_1 \sin \phi_1 = 0$$

$$\downarrow \quad \frac{V}{X_C} - \frac{V}{Z_L} \left(\frac{X_L}{Z_L} \right) \Rightarrow \frac{1}{X_C} = \frac{X_L}{Z_L^2}$$

$$Z_L^2 = X_L X_C = \omega L \left(\frac{1}{\omega C} \right)$$

$$Z_L^2 = \frac{L}{C} ; Z_L = \frac{L}{C}$$

$$Z_L^2 = \frac{L}{C}$$

$$Z_L = \sqrt{R^2 + X_L^2}$$

$$\therefore R^2 + X_L^2 = \frac{L}{C}$$

$$X_L^2 = \frac{L}{C} - R^2$$

$$X_L = \sqrt{\frac{L}{C} - R^2}$$

↓

$$\omega L$$

↓

$$2\pi f L = \sqrt{\frac{L}{C} - R^2}$$

$$f_o = \frac{1}{2\pi L} \sqrt{\frac{L}{C} - R^2} \quad (\text{or})$$

$$f_o = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

If $R=0$; $f_o = \frac{1}{2\pi} \sqrt{\frac{1}{LC}}$

$$\text{admittance} = \frac{1}{Z}$$

series $\frac{1}{Z} = \frac{1}{R} + j \frac{1}{X_C} \times \frac{j}{j}$ $j^2 = -1$

parallel $\frac{1}{Z} = \frac{1}{R} - \frac{1}{jX_C}$

$$\frac{1}{Z} = \frac{jX_C - R}{RjX_C}$$

$$Z = \frac{-RjX_C \times \frac{R+jX_C}{RjX_C}}{RjX_C} = \frac{R+jX_C}{CR}$$

$$Q_o = \frac{\omega L}{R}$$

$$Z = Z' - jZ''$$

$$\left(\frac{-RjX_C}{R^2 + X_C^2} + \frac{RjX_C}{R^2 + X_C^2} \right) =$$

$$Z' = \frac{R^2 X_C^2}{R^2 + X_C^2} - j \frac{R^2 X_C}{R^2 + X_C^2}$$

Q) The current seen in each branch of a two branched parallel circuit are given by the

expression : $i_A = 7.07 \sin(314t - \frac{\pi}{4})$



$$i_B = 21.2 \sin(314t + \frac{\pi}{3})$$

$$V = 354 \sin(314t)$$

Calculate the ohmic value of the component assuming that all the components are in pur state whether the reactive components are inductive or capacitive

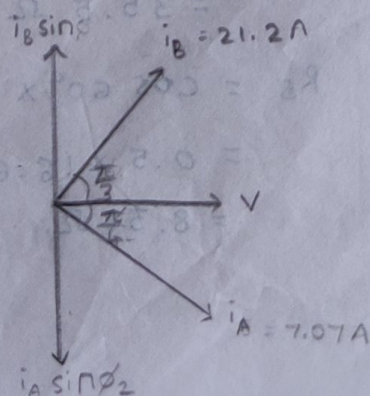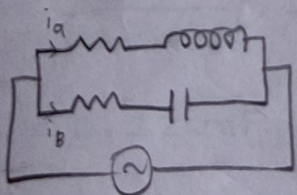A) Given :

$$i_A = 7.07 \sin(314t - \frac{\pi}{4})$$



$$\begin{aligned}
 X &= I_1 \cos \phi_1 + I_2 \cos \phi_2 \\
 &= 7.07 \cos 45^\circ + 21.2 \cos 60^\circ \\
 &= 7.07 \left(\frac{1}{\sqrt{2}} \right) + 21.2 \left(\frac{1}{2} \right) \\
 &= 15.6 \text{ A}
 \end{aligned}$$

$$\begin{aligned}
 Y &= 21.2 \sin 60^\circ - 7.07 \sin 45^\circ \\
 &= 21.2 \left(\frac{\sqrt{3}}{2} \right) - 7.07 \left(\frac{1}{\sqrt{2}} \right) \\
 &= 13.36 \text{ A}
 \end{aligned}$$

$$\begin{aligned}
 i &= \sqrt{X^2 + Y^2} \\
 &= \sqrt{(15.6)^2 + (13.36)^2} \\
 &= 20.53 \text{ A}
 \end{aligned}$$

$$\tan \phi = \frac{Y}{X} = \frac{13.36}{15.6} = 0.856$$

$$\phi = \tan^{-1}(0.856)$$

$$\boxed{\phi = 40.5^\circ}$$

$$Z_A = \frac{V}{I_A} = \frac{354}{7.07} = 50.07 \Omega$$

$$Z_B = \frac{V}{I_B} = \frac{354}{21.2} = 16.69 \Omega$$

WKT :

$$\cos \phi_A = \frac{R_A}{Z_A}$$

$$R_A = \cos \phi_A Z_A$$

$$= \cos 45^\circ \times 50.07$$

$$= 0.707 \times 50.07$$

$$= 35.5 \Omega$$

$$R_B = \cos 60^\circ \times 16.69$$

$$= 0.5 \times 16.69$$

$$= 8.34 \Omega$$

$$Z_A = \sqrt{R_A^2 + X_L^2}$$

$$(Z_A)^2 = (R_A)^2 + (X_L)^2$$

$$X_L^2 = (Z_A)^2 - (R_A)^2$$

$$X_L = \sqrt{(Z_A)^2 - (R_A)^2}$$

$$= \sqrt{(50.07)^2 - (35.5)^2}$$

$$= \sqrt{2507 - 1260.2}$$

$$= \sqrt{1246.8}$$

$$X_L = 35.3$$

↓

$$\omega L = 35.3$$

↓

$$314 L = 35.3$$

$$L = \frac{35.3}{314} = 0.112 \text{ H}$$

Similarly;

$$X_C = \sqrt{(Z_B)^2 - (R_B)^2}$$

$$= \sqrt{(16.69)^2 - (8.34)^2}$$

$$= \sqrt{278.5 - 69.5}$$

$$= \sqrt{209}$$

$$X_C = 14.45$$

↓

$$\frac{1}{\omega C} = 14.45$$

$$C = \frac{1}{314 \times 14.45} = \frac{1}{4537.3}$$

$$C = 0.22 \text{ mF}$$