

23Z102 - BASICS OF ELECTRICAL AND ELECTRONIC SYSTEMS

(BEES)

Unit 1 : DC Circuits

Unit 2 : AC Circuits

Unit 3 : Magnetic induction and circuits

Unit 4 : Semiconductor devices

Unit 5 : Operational Amplifiers (OP AMP)

DC CIRCUITS :

Components :

i) Resistors

Ohm's Law - $V = IR$ Unit of resistance - Ohm (Ω)

Resistors are made up of carbon, ceramic or metals


Power : $P = I^2 R = VI$

COLOR CODE :

BB R O Y G B V G W

Tolerance : Gold, Silver, Colourless

Resistance is independent of frequency.

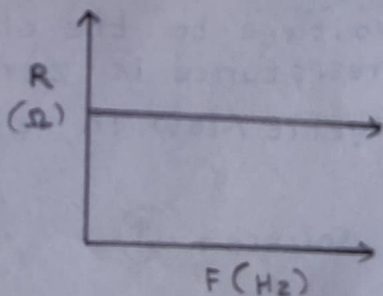

ii) Capacitors :

* Unit of Capacitance (C) = Farad (F)

* $1 \text{ F} = 96500 \text{ C}$

* $1 \text{ C} = 6.25 \times 10^{18}$

* Charge of electron = $1.6 \times 10^{-19} \text{ C}$

$$q = CV$$

$$C = \frac{EA}{d}$$

* Capacitance varies with frequency.

iii) Inductors :

* Inductance (L)

* Unit - Henry (H)

$$X_L = \omega L \text{ } (\Omega)$$

$$V = L \frac{dI}{dt}$$

*

Power Source :

i) Voltage source \oplus constant voltage to the circuit

ii) Current source

* Constant voltage to the circuit

* Internal resistance is zero for ideal cases and negligible / low in reality.

ii) Current source: \uparrow

* Constant current

* Internal resistance is open circuit for ideal case, and infinity for real cases.

Emf & Potential difference :

* Emf (Energy conversion)


* Potential difference (No energy conversion)

Resistors in series :

$$R = R_1 + R_2 + R_3$$

I is same

V is different

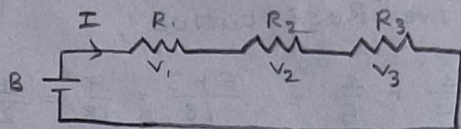

$$V = iR$$

$$V_1 = iR_1$$


$$\frac{V}{R} = \frac{V_1}{R_1} ; V_1 = V \frac{R_1}{R} ; \boxed{V_1 = V \frac{R_1}{R_1 + R_2 + R_3}}$$

Resistors in parallel :

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

I is different

V is same

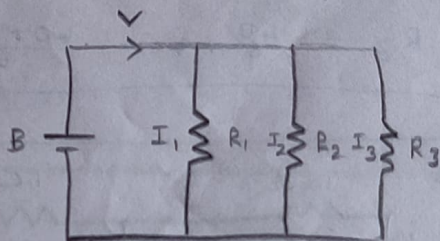

$$V = IR$$

$$V_1 = I_1 R_1$$


$$IR = I_1 R_1 ; I_1 = \frac{IR}{R_1} ; \boxed{I_1 = I \frac{R}{R_1}}$$

$$i \left[\frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} \right] = i_1 R_1$$

$$\boxed{i_1 = i \left(\frac{R_2 R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1} \right)}$$

5/9/24

1)

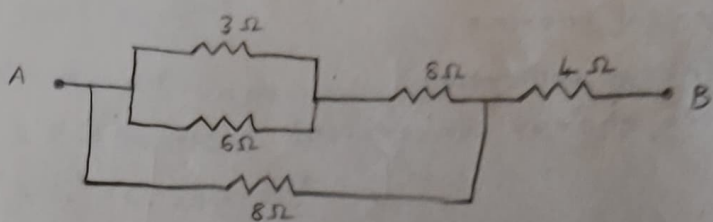

Effective Resistance;

$$\frac{1}{R} = \frac{1}{3} + \frac{1}{6} = \frac{6+3}{18} = \frac{9}{18} = \frac{1}{2}$$

$$R = 2 \Omega$$


$$R_1 = 2 \Omega + 8 \Omega = 10 \Omega$$

$$\frac{1}{R_2} = \frac{1}{10} + \frac{1}{8} = \frac{8+10}{80} = \frac{18}{80} = \frac{9}{40}$$

$$R_3 = \frac{5}{9} + \dots = \frac{5+36}{9} = 4 \frac{1}{9} \Omega$$

$$R_3 = \frac{40}{9} + 4 = \frac{40+36}{9} = \frac{76}{9} \Omega$$

2)

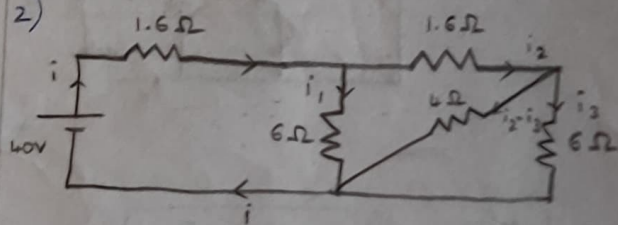

$$R_1 = 1.6 + 6 = 7.6 \Omega$$

$$\frac{1}{4} + \frac{1}{6} = \frac{6+4}{24} = \frac{10}{24} = \frac{5}{12}$$

$$\frac{12}{5} + 1.6 = \frac{12+8}{5} = \frac{20}{5} = 4$$

$$\frac{1}{4} + \frac{1}{6} = \frac{6+4}{24} = \frac{10}{24} = \frac{5}{12} = 2.4$$

$$2.4 + 1.6 = 4 \Omega$$

$$R_{eff} = 4 \Omega$$


$$\frac{3}{1.6} \times \frac{1.6}{2.0}$$

$$I = \frac{V}{R_{eff}}$$

$$I = \frac{40}{4}$$

$$I = 10 A$$

3)

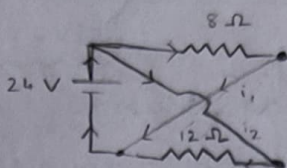

$$i_1 = \frac{V}{R_1} = \frac{24}{8} = 3 \text{ A}$$


$$i_2 = \frac{V}{R_2} = \frac{24}{12} = 2 \text{ A}$$

$$i = i_1 + i_2 = 5 \text{ A}$$

$$\frac{1}{R_{\text{eff}}} = \frac{1}{8} + \frac{1}{12} = \frac{12+8}{96} = \frac{20}{96} = \frac{5}{24}$$

$$\frac{24}{5} = 4.8$$
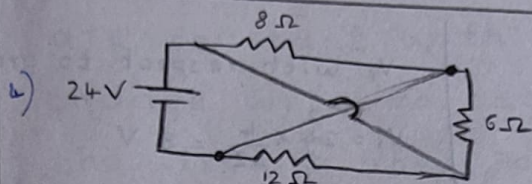
$$I = \frac{V}{R} = \frac{24}{\frac{24}{5}} = 5 \text{ A}$$




$$\frac{1}{R_{\text{eff}}} = \frac{1}{8} + \frac{1}{12} + \frac{1}{6} = \frac{72+48+96}{576} = \frac{216}{576}$$

$$R_{\text{eff}} = \frac{8}{3} \Omega$$

$$I = \frac{V}{R_{\text{eff}}} = \frac{24}{\frac{8}{3}} = 3 \times 3 = 9 \text{ A}$$

11/9/24

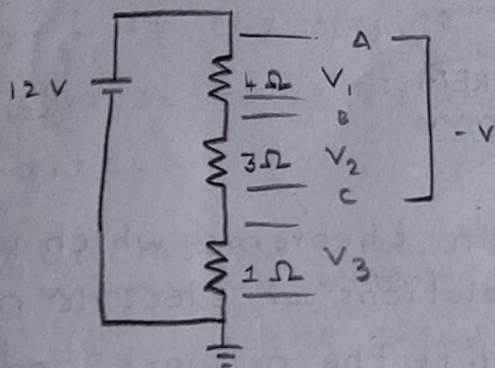

$$V_1 = V \times \frac{R_1}{R_1 + R_2 + R_3}$$

$$R_{\text{eff}} = 4 + 3 + 1 = 8 \Omega$$

$$V = IR$$

$$I = \frac{V}{R} = \frac{12}{8} = \frac{3}{2} = 1.5$$

$$V_1 = IR_1 = 1.5 \times 4 = 6$$


$$V_2 = IR_2 = 1.5 \times 3 = 4.5$$

$$V_3 = IR_3 = 1.5 \times 1 = 1.5$$

$$V = V_1 + V_2$$

$$= 6 + 4.5$$

$$= 10.5 \text{ V}$$

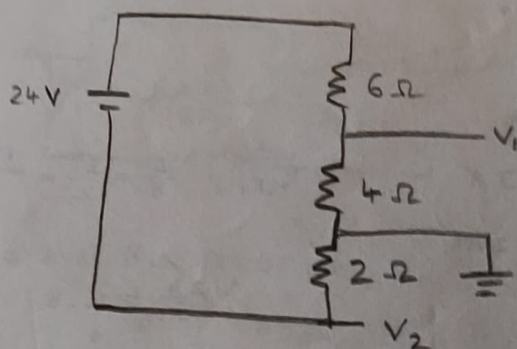

$$R_{\text{eff}} = 12 \Omega$$

$$I = \frac{V}{R} = \frac{24}{12} = 2 \text{ A}$$

$$V_1 = IR_1 = 2 \times 6 = 12 \text{ V}$$

$$V_2 = IR_2 = 2 \times 4 = 8 \text{ V}$$

$$V_2 = IR_3 = 2 \times 2 = 4 \text{ V}$$

V_1 with respect to ground.

$$V_1 = 24 \times \frac{4}{12} = 8 \text{ V}$$

$$V_2 = 24 \times \frac{2}{12} = -4 \text{ V} \quad (V_2 \text{ is at negative})$$

V_1 is positive with respect to ground.

V_2 is negative with respect to ground.

9/24 DEFINITIONS :

DC NETWORK THEOREM :

- * There are certain theorems which when applied to the solutions of electric network the theorem simplify the network and render their analytical solutions very easily. These theorems can also be applied to AC network where the impedance replace the ohmic resistance of DC systems.