

11/12/24

Unit 5

OPERATIONAL AMPLIFIERS

* OP-amp is a versatile building block that can be used for realising several electronic circuits.
 * Operational \rightarrow it performs mathematical operations.

* Amplifiers \rightarrow amplifies the input
 (Eg: $1\text{ V} \rightarrow 10^5\text{ V}$)
 10^5 times - amplification

* General OP-AMP \Rightarrow IC 741 with 8 pins.



* Out of 8, 7 pins are active)

* 8th pin is for balance

There are two inputs

-Inverting & Non-inverting

And one output

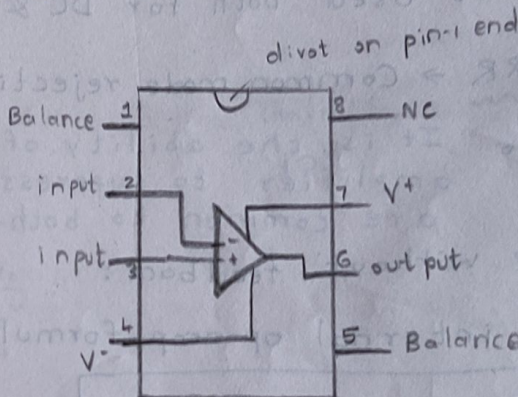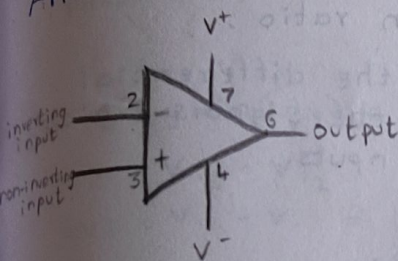

* This amplifier is called differential amplifier.

*

$$I_2 = 1\text{ V}$$

$$I_3 = 1.0001\text{ V}$$

$$0.0001 \times 10^5 = 100\text{ V} \otimes$$

$$= 15\text{ V}$$

$$I_2 = 1\text{ V}$$

$$I_3 = 1\text{ V}$$

$$0 \times 10^5 = 0\text{ V} \otimes \checkmark$$


$$= 15\text{ V}$$

15 \rightarrow Saturation voltage

* OP-AMP is highly unstable

* Output always = $+15$ (or) -15 .

Characteristics of The ideal op-amp:

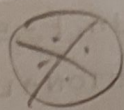

Examples.

- i) Infinite voltage gain:
 - * A voltage difference at the two inputs is magnified infinitely.
- ii) Infinite input impedance: \rightarrow In reality: $(10^6 \Omega)$ (or) $(M\Omega)$
 - * No current flows into inputs.
- iii) Zero output impedance:
 - * rock-solid independent of load.
 - * roughly true up to current maximum (5-25 mA).
- iv) Infinitely fast (infinite bandwidth):
 - * in truth, limited to few MHz range
 - * slow rate, limited to $0.5-20 V/\mu s$
response rate

OP-AMP is Used both for DC & AC currents,

- v) CMRR \rightarrow Common mode rejection ratio.
- ~~But~~ It is the ability of the differential amplifier to suppress the signals which are common to both inputs.

OP-amp without feedback:


- * The internal op-amp formula is;

$$V_{out} = \text{gain} \times (V_+ - V_-)$$


If V_+ is greater than V_- , output goes +
 $V_- > V_+$, output \Rightarrow -

* What other electronic circuits we give to op-amp is

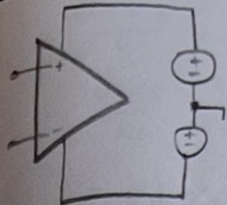
Current will flow outside the amplifier & not inside.



\Rightarrow

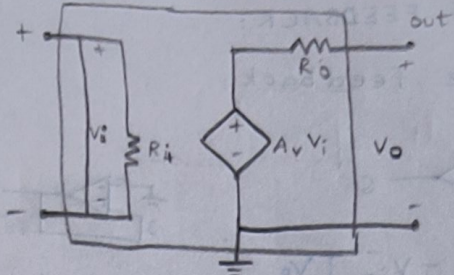

\Downarrow

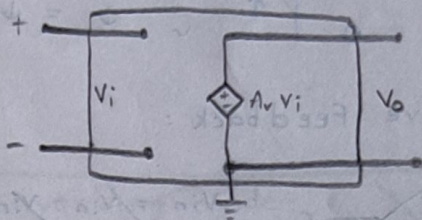

* $R_i \rightarrow \infty$; $R_o \rightarrow 0$

$= V_{CC} \text{ \& } -V_{EE} \text{ (} \sim \pm 5V \text{ to } \pm 15V \text{)}$

parameter

$V_o = \text{gain}(A_v) \times V_i$

$V_i = V_{i3} - V_{i2}$

$V_i = V_+ - V_- = \frac{V_o}{A_v}$

$\frac{V_o}{V_i} = A_v$; $V_o = A_v V_i$

Gain

10^4

If : $V_i = 0.1 \text{ mV}$

Broadly op-amp circuits can be divided in two;



- i) op-amp operating in linear region
- ii) op-amp operating in saturation region

Whether an op-amp in a given circuit will operate in linear (or) saturation region depends on ;

- i) input voltage magnitude
- ii) type of feedback (positive or negative)

OP-AMP FEEDBACK:

i) Positive feedback:

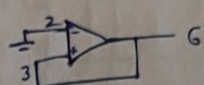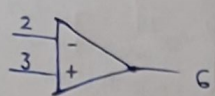


$$V_{in} = V_{in}^+ - V_{in}^- \quad \left| \quad V_o \right.$$

↑	↑	0	↑
↑	↑	0	↑

$$V_{in} = V_{in}^+ - V_{in}^- \quad \left| \quad V_o \right.$$


↓	↓	0	↓
↓	↓	0	↓

ii) Negative feedback:

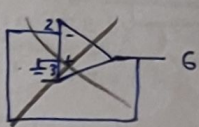

$$V_{in} = V_{in}^+ - V_{in}^- \quad \left| \quad V_o \right.$$


↓	↓	0	↑
↓	↓	0	↓

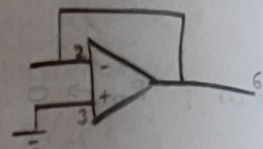

$$V_{in} = V_{in}^+ - V_{in}^- \quad \left| \quad V_o \right.$$

↑	= 0 - ↓	↑
↓	= 0 - ↓	↓
↓	= 0 - ↑	↓

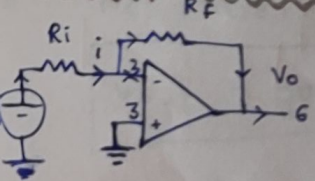* All op-amp negative feedback only will be used.
Op-amp operated in inverting mode:



$$i_{R_i} = \frac{0 - V_{in}}{R_i} = - \frac{V_{in}}{R_i}$$

$$i_{R_f} = \frac{V_o - 0}{R_f} = \frac{V_o}{R_f}$$

$$i = i_{R_i} = i_{R_f}$$

$$- \frac{V_{in}}{R_i} = \frac{V_o}{R_f}$$

Golden Rules:

- i) No current flows through op-amp.
- ii) If operating in negative feedback, the output will make sure that difference between two input voltage is zero.

$$V^+ - V^- = 0$$

virtual ground: When the terminal 3 is grounded, then 2 is also grounded

$$V_o = -V_{in} \frac{R_f}{R_i}$$

$$i_{R_i} = \frac{0 - V_{in}}{R_i} = -\frac{V_{in}}{R_i}$$

$$i_{R_f} = \frac{V_o - 0}{R_f} = \frac{V_o}{R_f}$$


$$i = i_{R_i} = i_{R_f}$$

$$-\frac{V_{in}}{R_i} = \frac{V_o}{R_f}$$

$$A_v = -\frac{R_f}{R_i}$$

$$V_o = -V_{in} \frac{R_f}{R_i}$$

Op-amp operated in non-inverting mode:

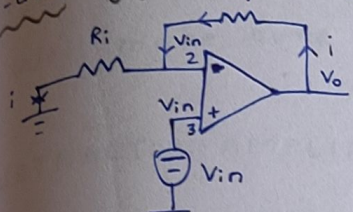

$$i_{R_i} = \frac{V_{in} - 0}{R_i}$$

$$i_{R_f} = \frac{V_o - V_{in}}{R_f}$$

$$i_{R_i} = i_{R_f}$$

$$\frac{V_{in}}{R_i} = \frac{V_o - V_{in}}{R_f}$$

$$\frac{V_o}{R_f} = V_{in} \left(\frac{1}{R_i} + \frac{1}{R_f} \right)$$

$$\frac{V_o}{R_f} = V_{in} \left[\frac{R_f + R_i}{R_i R_f} \right]$$


$$V_o = V_{in} R_f \left[\frac{R_f + R_i}{R_i R_f} \right] = V_{in} R_f \left[\frac{1}{R_i} + \frac{1}{R_f} \right] = V_{in} \left[1 + \frac{R_f}{R_i} \right]$$

$$V_o = V_{in} \left(1 + \frac{R_f}{R_i} \right)$$

$$A_v = 1 + \frac{R_f}{R_i}$$

Op-amp with capacitor in inverting mode:

(Differentiator):

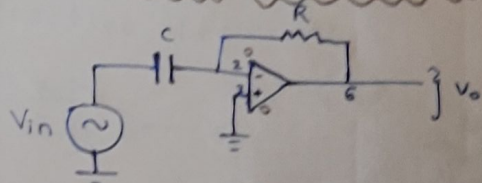

WKT:

$$q = C V_{in}$$

$$\frac{dq}{dt} = C \frac{dV_{in}}{dt}$$

$$i_c = C \frac{dV_{in}}{dt}$$

$$i_R = \frac{V_o}{R}$$

$$i = i_c = i_R$$


$$C \frac{dV_{in}}{dt} = \frac{V_o}{R} \rightarrow (1)$$

$$V_o = RC \frac{dV_{in}}{dt} \rightarrow (2)$$

If input is in sine wave, output will be cos wave.

This is form differential.

RC \rightarrow time constant.

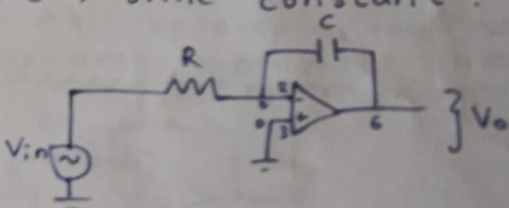

$$i_R = \frac{V_{in}}{R} = - \frac{V_{in}}{R}$$

$$i_R = - \frac{V_{in}}{R}$$

$$i_c = C \frac{dV_o}{dt}$$

$$i_c = i_R$$

$$C \frac{dV_o}{dt} = - \frac{V_{in}}{R}$$

$$dV_o = - \frac{1}{RC} V_{in} dt$$


$$V_o = - \frac{1}{RC} \int V_{in} dt$$

If input is sin, output = cos,

This is integral

5/12/24

SUMMING AMPLIFIER :

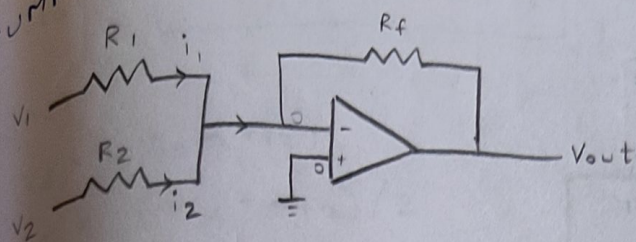

$$i_{Rf} = \frac{V_o}{R_f} \quad i_1 = \frac{0 - V_1}{R_1} = -\frac{V_1}{R_1}$$

$$\frac{V_{out}}{-R_f} = (V_1/R_1 + V_2/R_2) = \frac{V_o}{R_f} \quad i_2 = \frac{0 - V_2}{R_2} = -\frac{V_2}{R_2}$$


$$i_{in} = -\left(\frac{V_1}{R_1} + \frac{V_2}{R_2}\right)$$

If $R_1 = R_2$;
we get sum proportional to $V_1 + V_2$
then $i_{Rf} = i_{in}$;

$$V_o = -R_f \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} \right)$$

* We'll make our D/A converter this way.

SUBTRACTOR AMPLIFIER :

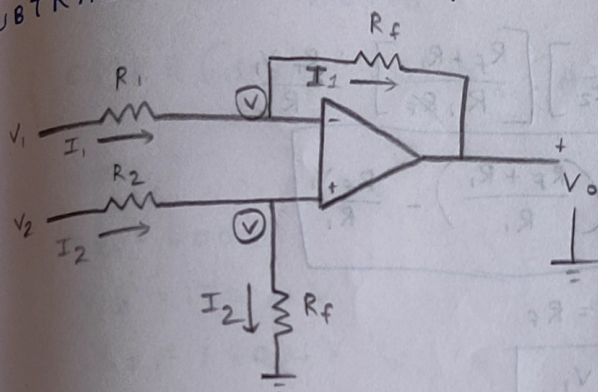

$$I_1 = \frac{V - V_1}{R_1} = \frac{V - V_o}{R_f} \quad I_2 = \left[\frac{V_2 - V}{R_2} \right] = \left[\frac{V - 0}{R_f} \right]$$

$$\frac{V_2 - V}{R_2} = \frac{V}{R_f}$$

$$\frac{V_2}{R_2} = \frac{V}{R_2} + \frac{V}{R_f}$$

$$\frac{V_2}{R_2} = V \left[\frac{1}{R_2} + \frac{1}{R_f} \right]$$

$$V = \frac{V_2}{R_2} \left/ \left(\frac{R_2 + R_f}{R_2 R_f} \right) \right.$$

$$V = \frac{V_2}{R_2} \left(\frac{R_f}{R_2 + R_f} \right)$$

$$V = V_2 \left(\frac{R_f}{R_2 + R_f} \right) \rightarrow \textcircled{1}$$

$$\frac{V_2 - V}{R_2} = \frac{V}{R_f}$$

$$V = \frac{R_f}{R_2} (V_2 - V)$$

$$V = \frac{R_f V_2}{R_2} - \frac{R_f V}{R_2}$$

$$V + \frac{R_f V}{R_2} = \frac{R_f V_2}{R_2}$$

$$V \left[1 + \frac{R_f}{R_2} \right] = \frac{R_f V_2}{R_2}$$

$$I_1 = \frac{V_i - V}{R_1} = \frac{V - V_o}{R_f}$$

$$\frac{V_i}{R_1} - \frac{V}{R_1} = \frac{V}{R_f} - \frac{V_o}{R_f}$$

$$\frac{V_o}{R_f} = \frac{V}{R_f} + \frac{V}{R_1} - \frac{V_i}{R_1}$$

$$\frac{V_o}{R_f} = V \left[\frac{1}{R_f} + \frac{1}{R_1} \right] - \frac{V_i}{R_1}$$

$$\frac{V_o}{R_f} = V \left[\frac{R_1 + R_f}{R_1 R_f} \right] - \frac{V_i}{R_1}$$

From (1); $V = V_2 \left[\frac{R_f}{R_2 + R_f} \right] \rightarrow \text{ⓧ}$

$$\frac{V_o}{R_f} \Rightarrow V_2 \left[\frac{R_f}{R_2 + R_f} \right] \left[\frac{R_1 + R_f}{R_1 R_f} \right] - \frac{V_i}{R_1}$$

$$V_o = V_2 \cancel{R_f} \left[\frac{R_f}{R_f + R_2} \right] \left[\frac{R_f + R_1}{R_1 \cancel{R_f}} \right] - \frac{R_f V_i}{R_1}$$

$$V_o = V_2 \left(\frac{R_f}{R_f + R_2} \right) \left(\frac{R_f + R_1}{R_1} \right) - \frac{R_f V_i}{R_1}$$

$$\text{If } R_1 = R_2 = R_f$$

$$V_o = V_2 - V_i$$

P-AMP CHARACTERISTICS :

Differential mode operation: (Difference should be amplified)

$$V_o = A_d V_i$$


A_d is typically very large



Common mode operation: (Common should be eliminated)

$$V_o = A_c V_i$$

$$A_c \ll A_d$$

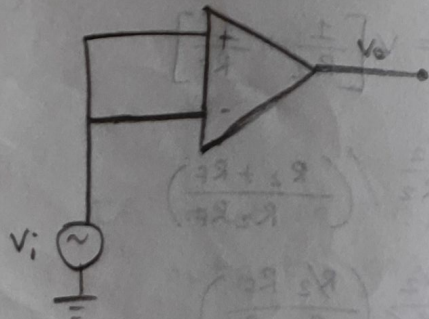

Output voltage:


$$\text{Total} = \boxed{V_o = A_d V_d + A_c V_c}$$

Where;

$$V_d = (V_{i1} - V_{i2})$$

$$V_c = (V_{i1} + V_{i2})/2$$

$$A_d \gg A_c$$

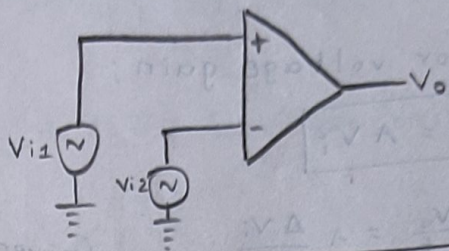

COMMON MODE REJECTION RATIO:

(Removes noise and amplifies the signal)

* The ratio of the differential gain to the common mode gain yields the common mode rejection ratio.

$$\text{CMRR} = A_d / A_c$$

$$\text{CMRR (dB)} = 20 \log_{10} (A_d / A_c)$$

Ex:

$$A_d = 4000$$

$$V_{i1} = 150 \mu V$$

$$V_{i2} = 140 \mu V$$

$$\text{CMRR} = a) 100 \quad b) 10^5$$

A) WKT:

$$V_d = (V_{i1} - V_{i2}) = (150 - 140) \mu V = 10 \mu V$$

$$V_c = \frac{V_{i1} + V_{i2}}{2} = \frac{150 + 140}{2} = \frac{290}{2} = 145 \mu V$$

WKT:

$$V_o = A_d V_d + A_c V_c = A_d V_d \left[1 + \frac{A_c V_c}{A_d V_d} \right]$$

$$\boxed{V_o = A_d V_d \left[1 + \frac{1}{\text{CMRR}} \left(\frac{V_c}{V_d} \right) \right]}$$

For CMRR = 1000

$$= 4000 * 10 \mu \left[1 + \frac{145 \mu}{100 * 10 \mu} \right] = 45.8 \text{ mV}$$

For CMRR = 10^5

$$= 4000 * 10 \mu \left[1 + \frac{145 \mu}{10^5 * 10 \mu} \right] = 40.006 \text{ mV}$$

To increase accuracy, we have increase CMRR value.

Ex: Slew rate = 2 V/s ,

$$\left(\frac{dV_o}{dt} \right)$$

what is the maximum closed-loop voltage gain that can be used when the input signal varies by 0.5 V in 10 s ?

A) For voltage gain;

$$V_o = A V_i$$

$$\frac{\Delta V_o}{\Delta t} = A \frac{\Delta V_i}{\Delta t}$$

$$\text{Given: } \frac{\Delta V_i}{\Delta t} = \frac{0.5}{10}$$

$$A = \frac{\frac{\Delta V_o}{\Delta t}}{\frac{\Delta V_i}{\Delta t}} = \frac{SR}{\frac{0.5}{10}} = \frac{2}{\frac{0.5}{10}} = \frac{20}{0.5} = \frac{200}{5} = 40$$