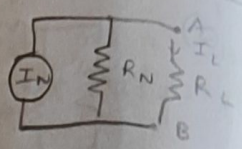



# NORTON'S THEOREM :



Steps :

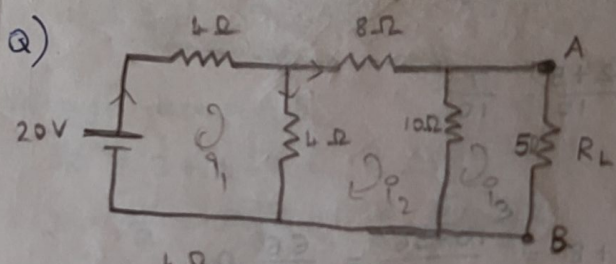- 1) Remove load resistance and short circuit terminals A and B.  $I_L = I_N \left( \frac{R_N}{R_N + R_L} \right)$
- 2) Find Norton current flowing through A and B.
- 3) Remove the short circuited A and B and replace all the power sources with their internal resistance.
- 4) Find Norton resistance ( $R_N$ ).
- 5) Draw the Norton equivalence resistance and find the current flowing through the load resistance. using ;

$$I_L = I_N \left( \frac{R_N}{R_N + R_L} \right)$$




(1/4)

$$\frac{1}{R} = \frac{1}{8} + \frac{1}{4} = \frac{4+8}{32} = \frac{12}{32}$$

$$R = \frac{32}{12} = \frac{16}{6} = \frac{8}{3} \Omega$$
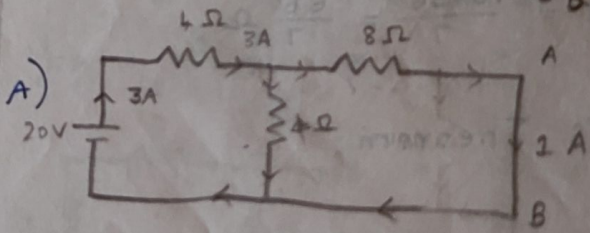
$$R = \frac{8}{3} + 4 = \frac{8+12}{3} = \frac{20}{3} \Omega$$




$$I = \frac{V}{R} = \frac{20}{\frac{20}{3}} = 3A$$

$$I_N = 3 \times \frac{4}{12} = 1A$$

~~$$\frac{1}{R} = \frac{1}{8} + \frac{1}{8} = \frac{1+8}{8} = \frac{9}{8}$$~~
~~$$I = \frac{V}{R} = \frac{20}{0.12} = 166.67A$$~~

$$I_N = 1A$$

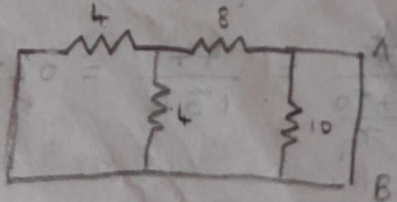

$$\frac{1}{R} = \frac{1}{4} + \frac{1}{4} = \frac{4+4}{16} = \frac{8}{16} = \frac{1}{2}$$

$$R = 2 + 8 = 10$$

$$\frac{1}{R} = \frac{1}{10} + \frac{1}{10} = \frac{2}{10}$$

$$R_N = \frac{10}{2}$$

$$\therefore I_L = I_N \left( \frac{R_N}{R_N + R_L} \right) = 1 \left( \frac{\frac{10}{2}}{\frac{10}{2} + 5} \right) = \frac{\frac{10}{2}}{\frac{20}{2} + 5} = \frac{5}{10 + 5} = \frac{5}{15} = \frac{1}{3}A$$