

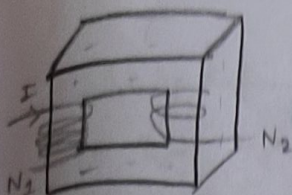


TRANSFORMER :

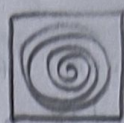

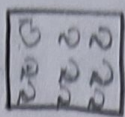Since transformer is static, the mechanical losses are nil.



Energy Losses in Transformer :

i) Copper Loss :

ii) Core Loss :

- * The core material should conduct magnetic flux (or) greater magnetic permeability (μ_r).

It should not conduct current.

* Eddy Current Loss :

- * Eddy currents are formed inside the transformer also due to $I^2 R$ energy is dissipated as heat.

- * To overcome this, laminated sheets are used which has air gaps and creates a resistance for the eddy currents and heat loss is reduced.

- * To increase resistance, Si is added as alloy to core material. (\because 3% Si is alloyed)

B) Hysteresis Loss :

- * In transformer, AC current at 50 Hz is used.
- * For every $\frac{1}{50}$ sec, the domains are oriented. polarity changes, the size of magnetic dipole increases & decreases vice
- * Due to change in orientations of domains, friction is produced, which generates heat.

- * To overcome this, soft-magnetic materials can be used.

For Ideal Transformer : Eddy current Loss & Hysteresis Loss will be zero.

Determination of Phase Angle and
in LCR Bridge:

$$Z = x + iy$$

$$Z_1 = x_1 + iy_1$$

$$r = |z| = \sqrt{x^2 + y^2}$$

$$Z_2 = x_2 + iy_2$$

$$\theta = \tan^{-1}\left(\frac{y}{x}\right)$$

$$Z = r \cos \theta + i \sin \theta$$

LCR : Two Frequencies:

100 Hz

1 kHz

$$C = 9.431 \mu F, \phi = -87.83^\circ$$

L

$$R = 9.812 k\Omega, \phi = 0.16^\circ$$

$$9.939 k\Omega, \phi = 0.03^\circ$$

Z

 ϕ

$$0.16^\circ$$

$$0.03^\circ$$

100 Hz

$$R = 9.812 k\Omega$$

$$\phi = 0.16^\circ$$

1000 Hz

$$R = 9.934 k\Omega$$

$$\phi = 0.03^\circ$$

RC:

$$C = 9.431 \mu F$$

$$\phi = -87.83^\circ$$

$$R \rightarrow 6.32 \Omega$$

$$Z \rightarrow 168.7 \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi \times 100 \times 9.431 \times 10^{-6}}$$

$$= 1.6884 \times 10^{-4} \times 10^6 = 168.84$$

RC:

$$C = 8.726 \mu F$$

$$\phi = -83.278^\circ$$

$$R = 2.151 \Omega$$

$$Z = 18.37 \Omega$$

$$Z = \sqrt{R^2 + (X_C)^2}$$

$$= \sqrt{39.94 + 2850}$$

$$= 168.11 \Omega$$

$$X_C = \frac{1}{2 \times 3.14 \times 1000 \times 8.726 \times 10^{-6}}$$

$$= 1.824 \times 10^{-5} \times 10^6$$

$$= 18.24$$

$$Z = \sqrt{(R)^2 + (X_C)^2} = \sqrt{(2.151)^2 + (18.24)^2}$$

$$= \sqrt{4.626 + 332.69}$$

$$= \sqrt{337.316}$$

$$= 18.36 \Omega$$

At 100 Hz : Pure Inductor;

At 1 kHz

$$L = 2.187 \text{ mH}$$

$$R = 9.859 \Omega$$

$$Z = 9.95 \Omega$$

$$\phi = 7.96^\circ$$

$$X_L = \omega L = 2\pi f L$$

$$= 2 \times 3.14 \times 100 \times 2.187 \times 10^{-3}$$

$$= 1373.4 \times 10^{-3}$$

$$= 1.373 \Omega$$


$$Z = \sqrt{(R)^2 + (X_L)^2}$$

$$L = 2.213 \text{ mH}$$

$$R = 2.151 \Omega \quad 9.896 \Omega$$

$$Z = 17.07 \Omega$$

$$\phi = 54.55^\circ$$

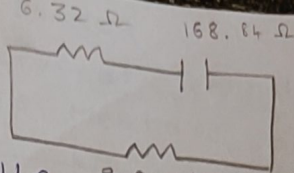

$$Z_1 = 168.11$$

96.04 -

RC || R
 $R = 100 \text{ Hz}$

$$Z_2 = 9.812 \times 10^3 \Omega$$

$$\left| \frac{1}{Z} \right| = \sqrt{\left(\frac{1}{Z_1} \right)^2 + \left(\frac{1}{Z_2} \right)^2}$$

$$= \sqrt{(5.948 \times 10^{-3})^2 + (0.1019 \times 10^{-3})^2}$$

$$= \sqrt{35.37 \times 10^{-6} + 0.01038 \times 10^{-6}}$$

$$= \sqrt{35.38 \times 10^{-6}}$$

$$\left| \frac{1}{Z} \right| = 5.94 \times 10^{-3}$$

$$Z = \frac{1}{5.94} \times 10^3 = 0.16835 \times 10^3 = 168.35 \Omega$$

$$Z_1 = 6.322 + i(168)$$

$$Z_2 = 9.812 \Omega + i(0)$$

$$\frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2} = \frac{Z_2 Z_1}{Z_1 + Z_2} =$$

Exp Value

RC:

$$Z = 168.5 \Omega$$

$$\phi = -86.88^\circ$$

RLC:

$$Z = 167.8 \Omega$$

$$\phi = -83.48^\circ$$

$$(x_1 + iy_1)(x_2 + iy_2)$$