

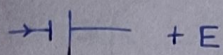


CONVENTIONS :

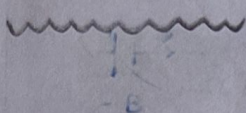

Ex :

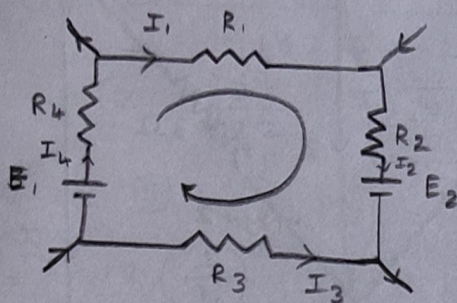

$$- I_1 R_1$$

$$- I_2 R_2$$

$$- E_2$$

$$+ I_3 R_3$$

$$+ E_1$$

$$- I_4 R_4$$

$$- I_1 R_1 - I_2 R_2 - E_2 + I_3 R_3 + E_1 - I_4 R_4 = 0$$

Gustave Robert Kirchhoff's

i) Current rule :

$$i_1 + i_2 + i_3 - i_4 = 0$$

" In any electrical network, the algebraic sum of the currents meeting at a junction is zero.

ii) Voltage rule :

"The algebraic sum of the products of current and resistance in each of the conductor in any closed path mesh in a network plus the algebraic sum of the emf in that path is equal to zero."


In

Battery :

* Current flows from positive to negative, the battery is discharging.

* Current flows from negative to positive, the battery is charging.

12.9.24

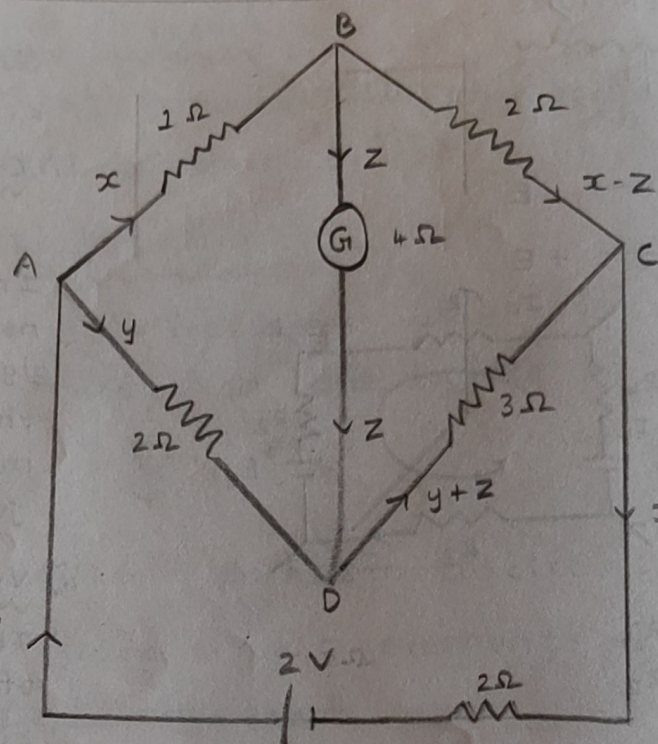

L1: (ADCA)

$$-2y - 3(y+z) - 2(x+y) + 2 = 0$$

$$-2y - 3y - 3z - 2x - 2y + 2 = 0$$

$$-2x - 7y - 3z + 2 = 0 \rightarrow \textcircled{1}$$

L2: (ABDA):

$$-x + 2y - 4z = 0 \rightarrow \textcircled{2}$$

L3: (ABCD A):

$$-x - 2(x-z) + 3(y+z) + 2y = 0$$

$$-x - 2x + 2z + 3y + 3z + 2y = 0$$

$$-3x + 5y + 5z = 0 \rightarrow \textcircled{3}$$

$$\textcircled{1} \Rightarrow -2x - 7y - 3z = -2$$

$$\textcircled{2} \times 2 \Rightarrow -2x + 4y - 8z = 0$$

$$\begin{array}{cccc} (+) & (-) & (+) & (-) \\ \hline & & & \end{array}$$

$$-11y + 5z = -2 \rightarrow \textcircled{4}$$

$$(2) \times 3 \Rightarrow -3x + 6y - 12z = 0$$

$$(3) \Rightarrow \begin{array}{r} -3x + 5y + 5z = 0 \\ (+) \quad (-) \quad (-) \\ \hline y - 17z = 0 \end{array} \rightarrow (5)$$

$$(4) \Rightarrow -11y + 5z = -2$$

$$(5) \times 11 \Rightarrow 11y - 187z = 0$$

$$+ 182z = +2$$

$$z = \frac{2}{182} ; \boxed{z = \frac{1}{91} A}$$

Sub in (5) ;

$$y - 17\left(\frac{1}{91}\right) = 0$$

$$\boxed{y = \frac{17}{91} A}$$

Sub in (2) ;

$$-x + 2\left(\frac{17}{91}\right) - 4\left(\frac{1}{91}\right) = 0$$

$$-91x + 34 - 4 = 0$$

$$+91x = +30$$

$$\boxed{x = \frac{30}{91} A}$$

$$i = x + y = \frac{30}{91} + \frac{17}{91} = \frac{47}{91} A$$

$$\text{Drop} = 2 \times 0.515 = 1.03$$

$$V = V - \text{Drop} = 2 - 1.03 = 0.97$$

$$R = \frac{V}{I} = \frac{0.97}{0.515} = 1.88 \Omega$$

$$x = 0.329$$

$$y = 0.186$$


$$z = 0.010$$

$$i = x + y$$

$$= 0.329 + 0.186$$

$$= 0.515 A$$

Q)

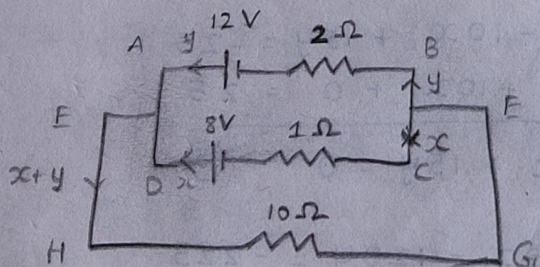

$$x = 3/4$$

$$y = 1.625$$

Loop : A D C B A:

$$+12 + 8 + x - 2y = 0$$

$$x - 2y = -4 \rightarrow (1)$$

Loop : E D C F G H E:

$$-8 + x + 10(x+y) = 0$$

$$11x + 10y = 8 \rightarrow (2)$$

$$(1) \times 5 \Rightarrow 5x - 10y = -20$$

$$(2) \Rightarrow 11x + 10y = 8$$


$$16x = -12$$

$$x = -\frac{12}{16}$$

$$\boxed{x = -\frac{3}{4}}$$

$$\text{Sub in (1): } 2y = -\frac{3}{4} + 4$$

$$\left(-\frac{3}{4}\right) - 2y = -4, 2y = \frac{-3+16}{2} = \frac{13}{2}$$

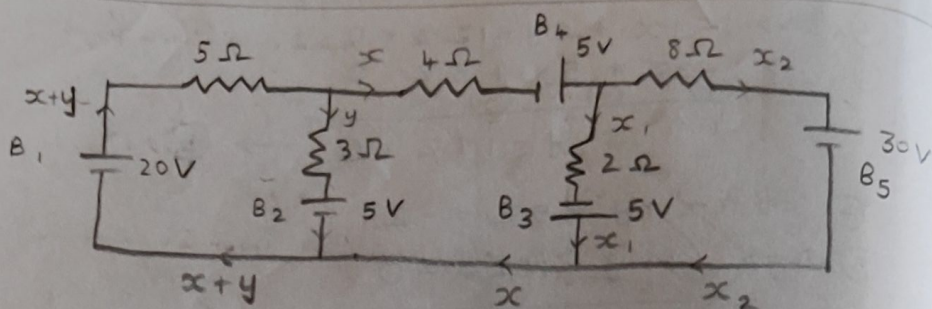

Loop 1.

$$20 - 5(x+y) - 3y - 5 = 0 ; \quad 20 - 5x - 5y - 3y - 5 = 0$$

$$-5x - 8y = -15 \rightarrow (1)$$

Loop 2 :

$$-4x + 5 - 2x_1 + 5 - 5 + 3y = 0$$

$$-4x - 2x_1 + 3y = -5 \rightarrow (2)$$

Loop 3 :

$$-8x_2 - 30 + 5 + 2x_1 = 0 \rightarrow (3)$$

$$2x_1 - 8x_2 - 25 = 0 \rightarrow (3)$$

Let $x_2 = x - x_1$

Sub in (3) ;

$$2x_1 - 8(x - x_1) - 25 = 0$$

$$2x_1 - 8x + 8x_1 - 25 = 0$$

$$-8x + 10x_1 = 25 \rightarrow (4)$$

$$(2) \times 5 \Rightarrow -20x - 10x_1 + 15y = -25$$

$$(4) \Rightarrow -8x + 10x_1 + 0 = 25$$

$$-28x + 15y = 0 \rightarrow (5)$$

$$(1) \times 15 \Rightarrow -75x - 120y = -225$$


$$(5) \times 8 \Rightarrow -224x + 120y = 0$$

$$+299x = +225 ; \quad x = \frac{225}{299}$$

Sub in (5) ;

$$-28\left(\frac{225}{299}\right) + 15y = 0$$
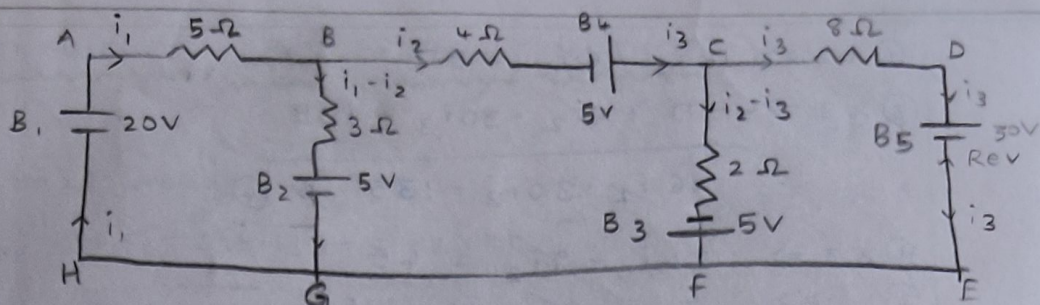
$$-6300 + 4485y = 0 ; \quad y = \frac{6300}{4485} ; \quad y = \frac{420}{299}$$



Battery :

$$B_1 \rightarrow i_1 \rightarrow 2.56 \text{ A (Discharging)}$$

$$B_2 \rightarrow i_1 - i_2 \rightarrow 0.74 \text{ A (Charging)}$$

$$B_3 \rightarrow i_2 - i_3 \rightarrow 4.96 \text{ A (Discharging)}$$

$$B_4 \rightarrow i_2 \rightarrow 1.82 \text{ A (Discharging)}$$

$$B_5 \rightarrow i_3 \rightarrow -3.13 \text{ A (Discharging)}$$

Loop 1) ABGHA :

$$-5i_1 - 3(i_1 - i_2) - 5 + 20 = 0$$

$$-5i_1 - 3i_1 + 3i_2 + 15 = 0$$

$$-8i_1 + 3i_2 = -15$$

$$8i_1 - 3i_2 = 15 \rightarrow \textcircled{1}$$

Loop 2) : BCFGB :

$$-4i_2 + 5 - 2(i_2 - i_3) + 5 + 5 + 3(i_1 - i_2) = 0$$

$$-4i_2 + 5 - 2i_2 + 2i_3 + 5 + 5 + 3i_1 - 3i_2 = 0$$

$$3i_1 - 9i_2 + 2i_3 = -15 \rightarrow \textcircled{2}$$

Loop 3) : CDEFC :

$$-8i_3 - 30 - 5 + 2(i_2 - i_3) = 0$$

$$-8i_3 - 35 + 2i_2 - 2i_3 = 0$$

$$2i_2 - 10i_3 = 35 \rightarrow \textcircled{3}$$

$$\textcircled{1} \times 2 \Rightarrow 16i_1 - 6i_2 = 30$$

$$\textcircled{3} \times 3 \Rightarrow 0 + 6i_2 - 30i_3 = 105$$

$$16i_1 - 30i_3 = 135 \rightarrow \textcircled{4}$$

$$\textcircled{1} \times 3 \Rightarrow 24i_1 - 9i_2 = 45$$

$$\textcircled{2} \Rightarrow \begin{array}{r} 3i_1 - 9i_2 + 2i_3 = -15 \\ (-) \quad (+) \quad (-) \quad (+) \end{array}$$

$$21i_1 - 2i_3 = 60 \rightarrow \textcircled{5}$$

$$\textcircled{4} \Rightarrow 16i_1 - 30i_3 = 135$$

$$\textcircled{5} \times 15 \Rightarrow 315i_1 - 30i_3 = 900$$

$$+299i_1 = +765$$

$$i_1 = \frac{765}{299} \quad (\text{or}) \quad i_1 = 2.55 \text{ A}$$

Sub in $\textcircled{1}$;

$$8i_1 - 3i_2 = 15$$

$$8\left(\frac{765}{299}\right) - 3i_2 = 15$$

$$6120 - 897i_2 = 4485$$

$$897i_2 = 1632$$

$$i_2 = \frac{1632}{897} \quad (\text{or}) \quad i_2 = 1.82 \text{ A}$$

Sub in $\textcircled{3}$;

$$2\left(\frac{1632}{897}\right) - 10i_3 = 35$$

$$3264 - 8970i_3 = 31395$$

$$-8970i_3 = 28131$$

$$i_3 = -\frac{28131}{8970}$$

$$i_3 = -3.13 \text{ A}$$