

18/9/24

MAXWELL'S LOOP CURRENT METHOD :

Loop 1): ABGHA :


$$-5i_1 - 3(i_1 - i_2) - 5 + 20 = 0$$

Loop 2): BCFG B :

$$-4i_2 + 5 - 2(i_2 - i_3) + 5 + 5 - 3(i_2 - i_1) = 0$$

Loop 3): CDEFC :

$$-8i_3 - 30 - 5 - 2(i_3 - i_2) = 0$$

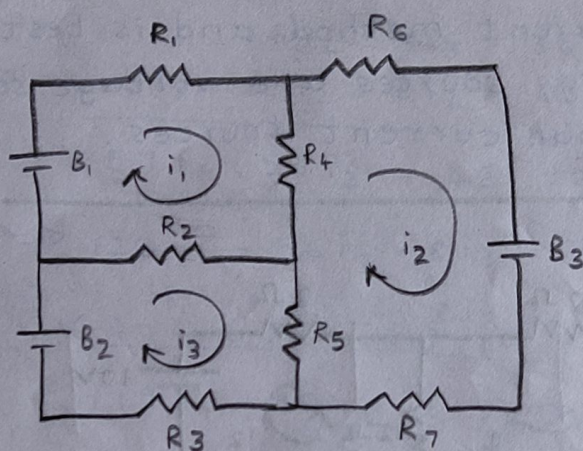

Loop 1 :

$$B_1 - i_1 R_1 - R_4(i_1 - i_2) - R_2(i_1 - i_3) = 0$$

Loop 2 :


$$-i_2 R_6 - B_3 - i_2 R_7 - R_5(i_2 - i_3) - R_4(i_2 - i_1) = 0$$

Loop 3 :

$$B_2 - R_2(i_3 - i_1) - R_5(i_3 - i_2) - i_3 R_3 = 0$$

MAXWELL'S LOOP CURRENT METHOD:

- * This method which is particularly well suited to coupled circuit solutions employs a system of loop or mesh currents instead of branch currents as in Kirchhoff's Law.
- * Here the current in different meshes are assigned continuous paths, so that they do not split at a junction into branch currents. This method eliminates a great deal of tedious work involved in the branch current method and is best suited when energy sources are voltage sources rather than current sources.

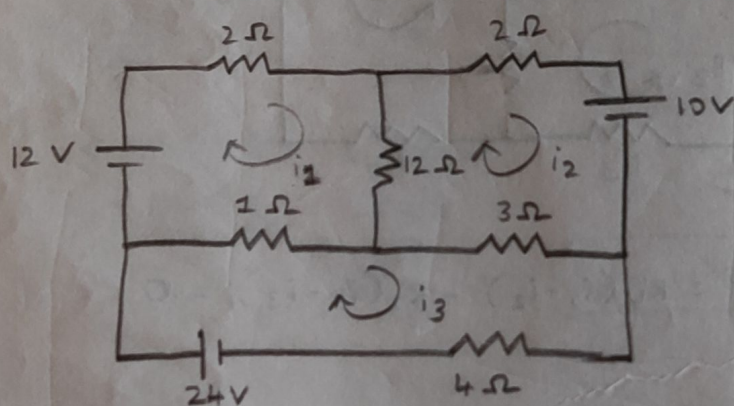

Loop 1:)

$$-2i_1 - 12(i_1 - i_2) - 1(i_1 - i_3) + 12 = 0$$

$$-2i_1 - 12i_1 + 12i_2 - i_1 + i_3 + 12 = 0$$

$$-15i_1 + 12i_2 + i_3 = -12$$

$$(x-) \quad 15i_1 - 12i_2 - i_3 = 12 \rightarrow (1)$$

Loop 2:)

$$-2i_2 - 10 - 3(i_2 - i_3) - 12(i_2 - i_1) = 0$$

$$-2i_2 - 10 - 3i_2 + 3i_3 - 12i_2 + 12i_1 = 0$$

$$12i_1 - 17i_2 + 3i_3 = 10 \rightarrow (2)$$

Loop 3:)

$$-1(i_3 - i_1) - 3(i_3 - i_2) - 4i_3 + 24 = 0$$

$$+i_3 + i_1 - 3i_3 + 3i_2 - 4i_3 + 24 = 0$$

$$i_1 + 3i_2 - 8i_3 = -24 \rightarrow (3)$$

$$(1) \times 3 \Rightarrow 45i_1 - 36i_2 - 3i_3 = 36$$

$$(2) \Rightarrow 12i_1 - 17i_2 + 3i_3 = 10$$

$$57i_1 - 53i_2 = 46 \rightarrow (4)$$

$$(1) \times 8 \Rightarrow 120i_1 - 96i_2 - 8i_3 = 96$$

$$(3) \Rightarrow \begin{array}{r} i_1 + 3i_2 - 8i_3 = -24 \\ (-) \quad (-) \quad (+) \quad (+) \end{array}$$

$$119i_1 - 99i_2 = 120 \rightarrow (5)$$


$$i_1 = -2.72 \text{ A}$$

$$i_2 = -2.05 \text{ A}$$

Sub in (3):


$$2.72 + 3(2.05) - 8i_3 = -24$$

$$i_3 = 4.11 \text{ A}$$

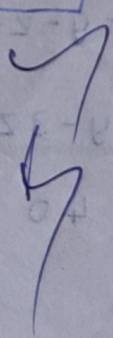

9/9/24

Q)

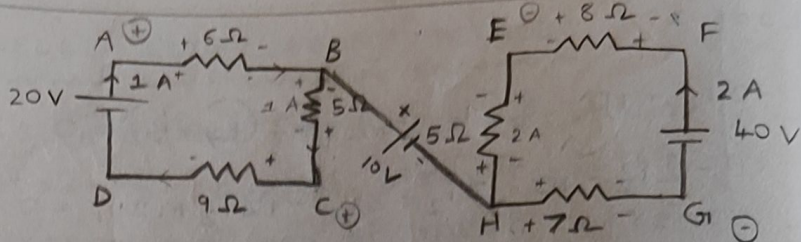

$$V_{CE} = ?$$

$$V_{AG} = ?$$

$$R_{eff} = 6 + 5 + 9 = 20 \Omega$$

$$I = \frac{V}{R_{eff}} = \frac{20}{20} = 1 A$$

$$R_{eff} = 8 + 5 + 7 = 20 \Omega$$

$$I = \frac{V}{R_{eff}} = \frac{40}{20} = 2 A$$

$$V_{CE} = -10V + 10V - 5V$$

$$V_{CE} = -5V$$

(\therefore change the Terminal)


C^{\ominus}, E^{\oplus}

$$V_{AG} = 6V + 10V + 14V$$

$$= 30V$$

($\therefore A^{\oplus}, G^{\ominus}$)

Q)

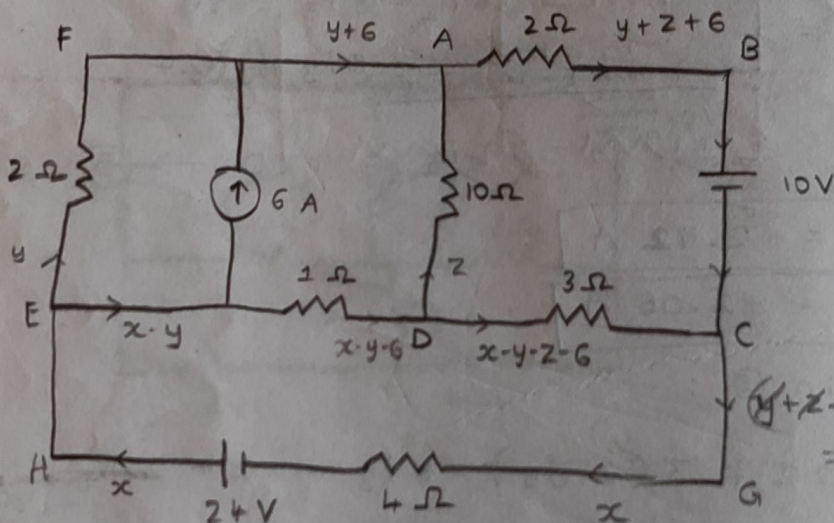

Loop 1: ABCDA :

$$-2(y+z+6) + 10 + 3(x-y-z-6) - 10z = 0$$

$$-2y - 2z - 12 - 10 + 3x - 3y - 3z - 18 - 10z = 0$$

$$3x - 5y - 15z = 40 \rightarrow \textcircled{1}$$

Loop 2: (FADEF):

$$+10(\cancel{y}Z) + 1(x - y - 6) - 2y = 0$$

$$10Z + x - y - 6 - 2y = 0$$

$$x - 3y + 10Z = 6 \rightarrow (2)$$

Loop 3: (ECGHE)

$$-1(x - y - 6) - 3(x - y - Z - 6) - 4x + 24 = 0$$

$$-x + y + 6 - 3x + 3y + 3Z + 18 - 4x + 24 = 0$$

$$-8x + 4y + 3Z = -48 \rightarrow (3)$$

Solving (1) (2) & (3);

$$x = 4.102 \text{ A}$$

$$y = -3.214 \text{ A}$$

$$Z = -0.774 \text{ A}$$

SUPERPOSITION THEOREM:

* Circuit should have more than one loop and more than one emf.

Steps:

